#### E-textile workshop for Fabricademy 2022/23

#### Jessica Stanley



### Today's workshop: e-textile continuity tester

What: simple circuit for testing whether two parts of a circuit are connected

Why: a handy tool to help you test your e-textile circuits

- Check that parts that should be connected actually are
- Find short circuits, i.e. parts that are connected but shouldn't be



#### **Background – tools for e-textiles**







Conventional electronic tools can be adapted for e-textiles, but aren't designed for them



Pictured: Pin Probes + Clip Probe by Irene Posch. DIY instructions at <u>http://www.ireneposch.net/tooling/</u> Further information: <u>https://www.stitchingworlds.net/exper</u> <u>imentation/tools-for-practitioners/</u> Irene Posch, Ebru Kurbak, Kobakant

## **Background – tools for e-textiles**

Other examples building on the same concept:

Safety pin crocodile clips for etextiles, Rachel Freire https://www.instructables. com/Safety-Pin-Crocodile-Clipsfor-ETextiles/





Pin connectors, Afroditi Psarra https://afroditipsarra.com/work /embodied-rf-ecologies



Threadboard, Chris Hill https://www.instructables.com/ The-ThreadBoard-V2-E-Textile-Prototyping-Board/

## **Step 1: getting started**

- It's a good idea to sketch your circuit design before you start sewing (to catch any mistakes *before* you sew them
- Choose your fabric and cut a piece large enough to hold the LED and battery
- If using a through-hole (standard)
  LED, use a pliers to twist the legs into coils to make it sewable



### Step 2: sewing the first conductive tracks

- Use conductive thread to stitch two conductive tracks
  - One from the LED to the edge of the fabric
  - Another from the edge of the fabric to under where the battery will go
- Make sure to sew these tracks separately, don't join them!
- When stitching the LED onto the fabric, stitch several times, tightly.



# Step 3: making the battery holder (option 1)

To make a battery holder from a strip of fabric:

- Cut a fabric strip slightly longer than the battery, and stitch one end of it to the fabric
- Then stitch a conductive thread track from the LED to the fabric strip. Make sure not to cross over these stitches with the stitches sewn in the previous step
- Place the battery under the fabric strip and stitch the other side of the fabric strip down. Make this as tight as possible!





# Step 3: making the battery holder (option 2)

To make a battery holder out of a safety pin:

- Put the battery in place and put the safety pin on top of it. Use regular (non-conductive) thread to stitch in place. Make stitches tight so that the safety pin presses against the battery.
- Use conductive thread to stitch a conductive thread track from the LED to the safety pin, making sure not to touch the conductive thread tracks sewn in Step 2.



### **Step 4: Making the probes**

- Use more conductive thread to make soft wires that are stitched to the conductive tracks on the fabric, and the safety pins
- Make sure all stitches are tight
- Going further: insulate the probe 'wires' by adding a nonconductive coating
- Other options: use alligator clips or insulated wire instead of conductive thread, or pins / other metal clips instead of safety pins



## Step 5: Test!

- Touch / pin the safety pins to a conductive fabric and the LED should light up
- Pin the safety pins to either side of a soft switch: the LED should light when the switch is closed
- Troubleshooting: if your circuit isn't working, check:
  - That your battery hasn't run out of charge
  - For any loose connections, or short circuits where things that shouldn't be joined are touching

